

Sequence Detector

Post Lab Assignments:

1. Beginner: Design a sequence detector for detecting the same sequence 1101 without overlapping.
2. Intermediate: There is a lock whose key is a sequence – 492156. Design an FSM based circuit.
3. Advanced: Design an FSM for a Traffic light controller for a road with simple T-point junction.