

Pre-Lab Quiz:

1. How many flip-flops do you need to implement an N-bit counter?
 - $N/2$ for even N, $(N+1)/2$ for odd N
 - N^2
 - 1
 - N
2. Synchronous construction reduces the delay time of a counter to the delay of:
 - all flip-flops and gates
 - all flipflops and gates after a 3 count
 - a single gate
 - a single flip-flop and a gate
3. What is the difference between combinational logic and sequential logic?
 - Combinational circuits are not triggered by timing pulses, sequential circuits are triggered by timing pulses.
 - Combinational and sequential circuits are both triggered by timing pulses.
 - Neither circuit is triggered by timing pulses.
4. A BCD counter is a _____?
 - binary counter
 - full-modulus counter
 - decade counter
 - divide-by-10 counter
5. When two counters are cascaded, the overall MOD number is equal to the _____ of their individual MOD numbers?
 - product
 - sum
 - log
 - reciprocal