

# **Traffic Light Controller**

## **Post Lab Assignments:**

1. Intermediate: Design a traffic light controller for two way operation and also allowing traffic to turn right and left.
2. Advanced: Design a lift controller using an FSM.